



CS 221 LOGIC DESIGN

Fall 2021

By Wessam El-Behaidy & Salwa Osama

1

MIDTERM EXAM

- Midterm Exam (based on announced schedule)

Day: Wed. 24 Nov.

Time: from 11 for Group1 (800 students)
from 12 for Group2 (395 students)



تنبيهات هامة

- الحضور للكلية قبل الموعد بنصف ساعة على الأقل
- يتواجد معك (قلم جاف- قلم رصاص – استيكة)
- الاجابة فى ورقة الاجابات الالكترونية بالقلم الرصاص وتحبر فى النهاية
- كتابة البيانات على ورقة الاسئلة وورقة الاجابة
- تسليم كلا من ورقة الاسئلة وورقة الاجابة (عدم تسليم الورقتين يلغى امتحانك)
- غير مسموح باستخدام الالة الحاسبة داخل الامتحان

الشكل العام لورقة التصحيح الألكتروني

الجنة الإعداد

Name: _____ Student ID: _____

Academic Year: 1 2 3 4 5




Department: _____

Subject: _____

Examination Form: A B C D E

Date: _____

Use pencil or blue or black pen

Fill the circle completely
(like this  Not like these  )

Do not fill in more than one circle

To change your answer use the eraser

DO NOT USE THE CORRECTOR

For true & False questions,
(mark (A) for true & (E) for false)

حتم الكترول

1 - A B C D E	11 - A B C D E	21 - A B C D E	31 - A B C D E	41 - A B C D E
2 - A B C D E	12 - A B C D E	22 - A B C D E	32 - A B C D E	42 - A B C D E
3 - A B C D E	13 - A B C D E	23 - A B C D E	33 - A B C D E	43 - A B C D E
4 - A B C D E	14 - A B C D E	24 - A B C D E	34 - A B C D E	44 - A B C D E
5 - A B C D E	15 - A B C D E	25 - A B C D E	35 - A B C D E	45 - A B C D E
6 - A B C D E	16 - A B C D E	26 - A B C D E	36 - A B C D E	46 - A B C D E
7 - A B C D E	17 - A B C D E	27 - A B C D E	37 - A B C D E	47 - A B C D E
8 - A B C D E	18 - A B C D E	28 - A B C D E	38 - A B C D E	48 - A B C D E
9 - A B C D E	19 - A B C D E	29 - A B C D E	39 - A B C D E	49 - A B C D E
10 - A B C D E	20 - A B C D E	30 - A B C D E	40 - A B C D E	50 - A B C D E
51 - A B C D E	61 - A B C D E	71 - A B C D E	81 - A B C D E	91 - A B C D E
52 - A B C D E	62 - A B C D E	72 - A B C D E	82 - A B C D E	92 - A B C D E
53 - A B C D E	63 - A B C D E	73 - A B C D E	83 - A B C D E	93 - A B C D E
54 - A B C D E	64 - A B C D E	74 - A B C D E	84 - A B C D E	94 - A B C D E
55 - A B C D E	65 - A B C D E	75 - A B C D E	85 - A B C D E	95 - A B C D E
56 - A B C D E	66 - A B C D E	76 - A B C D E	86 - A B C D E	96 - A B C D E
57 - A B C D E	67 - A B C D E	77 - A B C D E	87 - A B C D E	97 - A B C D E
58 - A B C D E	68 - A B C D E	78 - A B C D E	88 - A B C D E	98 - A B C D E
59 - A B C D E	69 - A B C D E	79 - A B C D E	89 - A B C D E	99 - A B C D E
60 - A B C D E	70 - A B C D E	80 - A B C D E	90 - A B C D E	100 - A B C D E

البيانات الأساسية



Name :

Academic Year : ☒ 1 ☐ 2 ☐ 3 ☐ 4 ☐ 5 مثال:
1st level

Department :

Subject:

Examination Form : ☐ A ☒ B ☐ C ☐ D ☐ E مثال:
Model B

Date :







رقم الطالب

مثال:

رقم الجلوس : 20187

Student ID									
2	0	1	8	7					
0	<input checked="" type="radio"/>	0	0	0	0	0	0	0	0
1	1	<input checked="" type="radio"/>	1	1	1	1	1	1	1
<input checked="" type="radio"/>	2	2	2	2	2	2	2	2	2
3	3	3	3	3	3	3	3	3	3
4	4	4	4	4	4	4	4	4	4
5	5	5	5	5	5	5	5	5	5
6	6	6	6	6	6	6	6	6	6
7	7	7	7	<input checked="" type="radio"/>	7	7	7	7	7
8	8	8	<input checked="" type="radio"/>	8	8	8	8	8	8
9	9	9	9	9	9	9	9	9	9

تعليمات هامة

- Use pencil or blue or black pen
- Fill the circle completely
(like this  Not like these   )
- Do not fill in more than one circle
- To change your answer use the eraser
- DO NOT USE THE CORRECTOR
- For true & False questions,
(mark (A) for true & (E) For false)



مثال لإجابات مظلة بشكل صحيح

مثال:
اجابة
السؤال
الأول
B

1 - <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	11 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	21 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	31 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	41 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
2 - <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	12 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	22 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	32 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	42 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
3 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D <input type="radio"/> E	13 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	23 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	33 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	43 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
4 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	14 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	24 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	34 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	44 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
5 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	15 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	25 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	35 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	45 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
6 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	16 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	26 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	36 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	46 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
7 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	17 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	27 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	37 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	47 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
8 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	18 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	28 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	38 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	48 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
9 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	19 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	29 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	39 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	49 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
10 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	20 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	30 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	40 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	50 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
51 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	61 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	71 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	81 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	91 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E
52 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	62 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	72 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	82 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E	92 - <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E

مثال لإجابات مظلة بشكل خطأ

	T	F		T	F		T	F
1 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	11 -	(A) (B) (C) (D) (E)	21 -	(A) (B) (C) (D) (E)	
2 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	12 -	(A) (B) (C) (D) (E)	22 -	(A) (B) (C) (D) (E)	
3 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	13 -	(A) (B) (C) (D) (E)	23 -	(A) (B) (C) (D) (E)	
4 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	14 -	(A) (B) (C) (D) (E)	24 -	(A) (B) (C) (D) (E)	
5 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	15 -	(A) (B) (C) (D) (E)	25 -	(A) (B) (C) (D) (E)	
6 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	16 -	(A) (B) (C) (D) (E)	26 -	(A) (B) (C) (D) (E)	
7 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	17 -	(A) (B) (C) (D) (E)	27 -	(A) (B) (C) (D) (E)	
8 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	18 -	(A) (B) (C) (D) (E)	28 -	(A) (B) (C) (D) (E)	
9 -	<input checked="" type="radio"/>	<input checked="" type="radio"/>	(B) (C) (D) (E)	19 -	(A) (B) (C) (D) (E)	29 -	(A) (B) (C) (D) (E)	

INSTRUCTIONS OF THE EXAM

Faculty of Computers and Artificial Intelligence
 CS 221: Logic Design
 Fall 2021- 2022 Time: 30 minutes
 Dr. Wessam El-Behaidy & Dr. Salwa Osama

MIDTERM EXAM (Group2_Model A)




Please read the following instructions carefully:

- ❖ Remember to **fill in your Name and Student ID**. Only sheets with both a name and ID will be graded.
- ❖ **Deliver both external answer sheet and the question paper**. If not, your paper will not graded
- ❖ **No Calculator** is permitted
- ❖ This is a **closed-book exam**. You are forbidden from accessing any external material, notes, electronic material, or online resources.

Name: ID:

- ❖ Attempt to **answer ALL** questions in this exam.

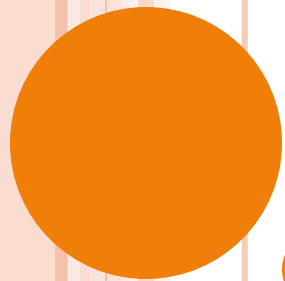Multiple choice Questions (Circle only **ONE** answer per question on the external answer sheet. If more than one answer is selected, the question will NOT be graded.) [20 marks]



11




COMBINATIONAL CIRCUITS

Lecture 6

REMEMBER

- This chapter includes the most important standard combinational circuits:
 - Adders, Subtractors, Decoders, Encoders, Multiplexers and Demultiplexer.
- We will know their internal design and the functionality of each.
- But, remember **our aim is to know how to think to design a circuit**

DECODERS

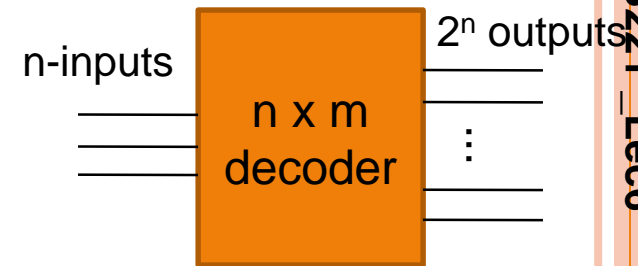


○ A Decoder:

- Is a popular combinational logic building block
- It converts input binary number to one high output


○ 2-input decoder

➔ Has four possible input binary numbers

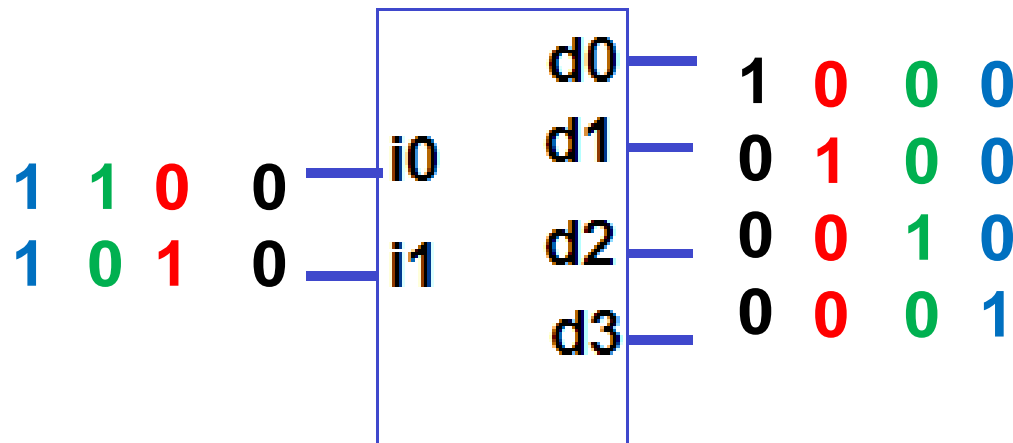➔ So, it has four outputs, one for each possible input binary number



DECODERS

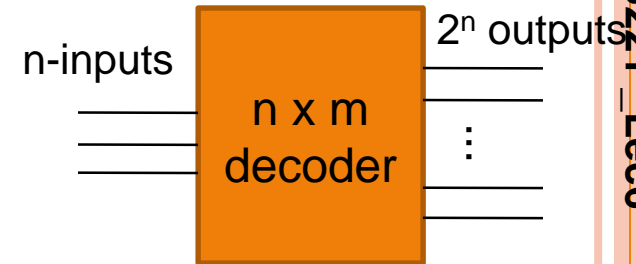

- Decoders are called *n-to-m* line decoders, where $m \leq 2^n$.
- A particular application of this decoder is:
Binary-to-octal conversion;
 - inputs : binary representation and
 - outputs : its correspondence in octal representation.

3-TO-8 LINE DECODER

3 input variables =? outputs

→ $2^3=8$ outputs

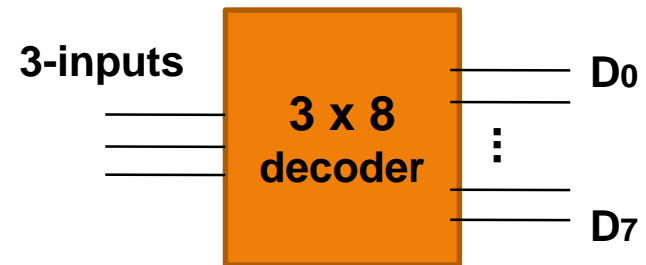


Table 4.6

Truth Table of a Three-to-Eight-Line Decoder

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃	<i>D</i> ₄	<i>D</i> ₅	<i>D</i> ₆	<i>D</i> ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


$D_0 = x'y'z'$,
 $D_4 = xy'z'$

$D_1 = x'y'z$,
 $D_5 = xy'z$

$D_2 = x'yz'$,
 $D_6 = xyz'$

$D_3 = x'yz$,
 $D_7 = xyz$

DECODERS

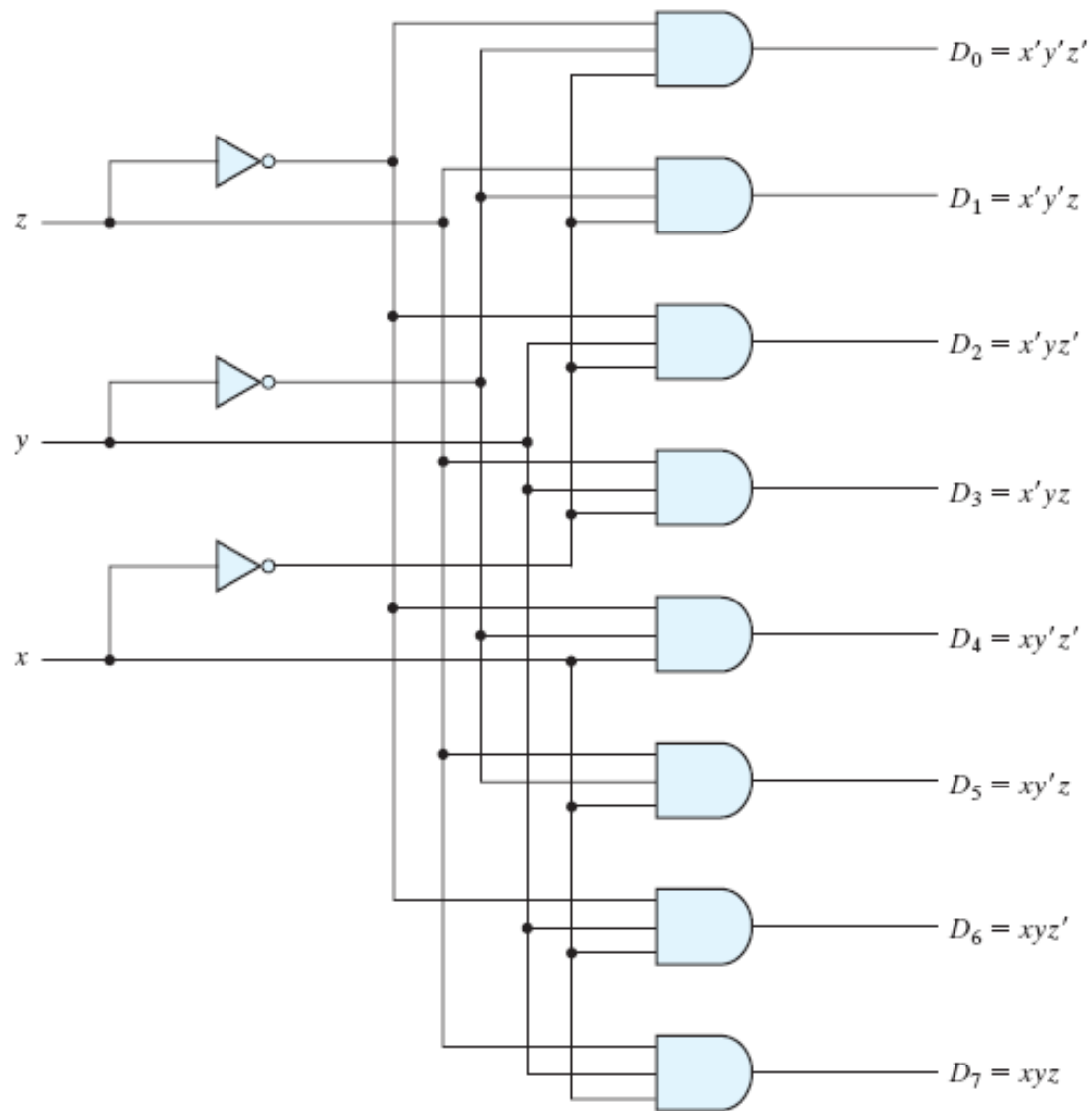


The output whose value is equal to 1 represents ***the minterm*** equivalent of the binary number currently available in the input lines


DECODER WITH ENABLE INPUT

Decoder with enable E

– if E=0, Outputs all 0

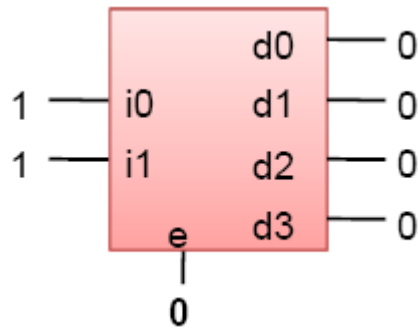

– if E=1, Regular behavior

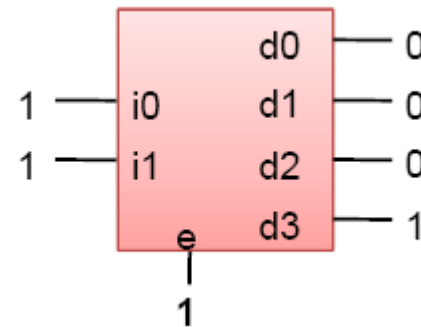


E	i0	i1	d0	d1	d2	d3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1		1		
1	1	0			1	
1	1	1				1

How to use as a block

4-TO-16 LINE DECODER

The 4-to-16 line decoder with two 3-to-8 line decoder with enable inputs

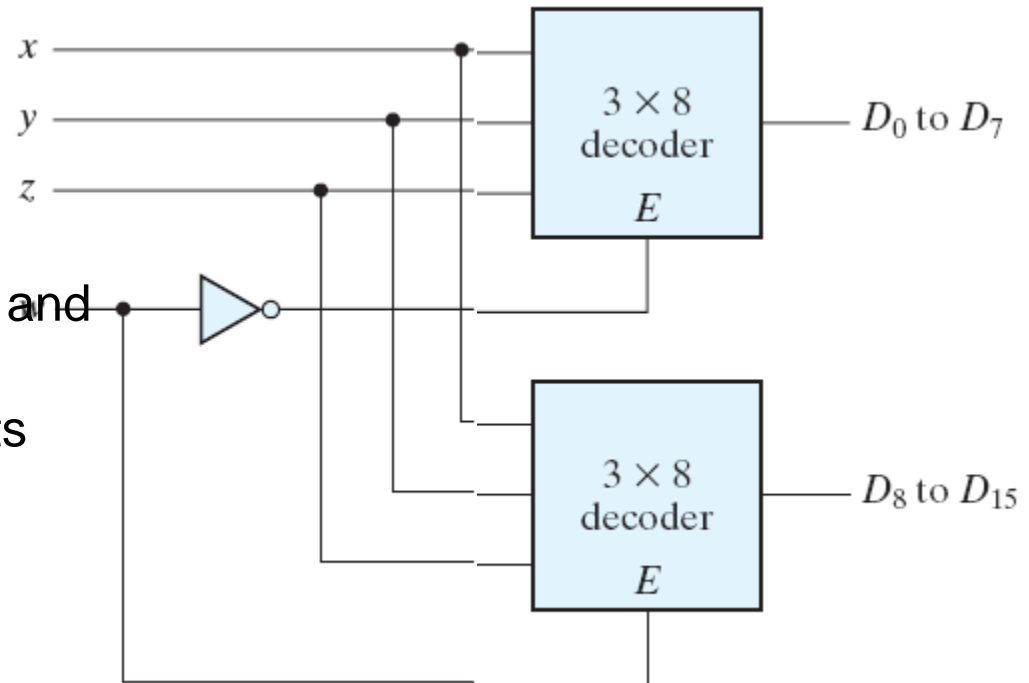- When $w=0$,
 - the top decoder is enabled and the other is disabled
 - The bottom decoder outputs all 0's and the top eight outputs generate minterms 0000 to 0111
- When $w=1$,
 - the bottom decoder is enabled and the other is disabled
 - The top decoder outputs all 0's and the bottom eight outputs generate minterms 1000 to 1111



BOOLEAN FUNCTION IMPLEMENTATION


- Since any Boolean function can be expressed in sum of minterms form:

→ A decoder with an external OR gate provides an implementation of the function

- Ex: Full-adder functions

$$S(x,y,z) = \Sigma(1,2,4,7)$$

$$C(x,y,z) = \Sigma(3,5,6,7)$$

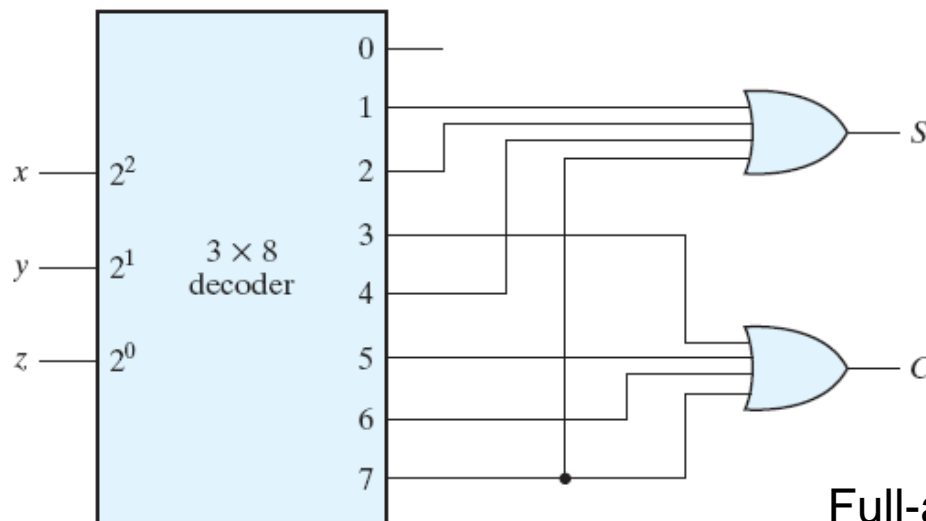


Full-adder with a decoder

NOTES

- A function with a long list of minterms requires an OR gate with large number of inputs
 - If the number of minterms $> 2^n/2$, then F' can be expressed with fewer minterms
 - In this case, NOR gate is used. Since the sum is complemented and the normal output is generated

ENCODERS

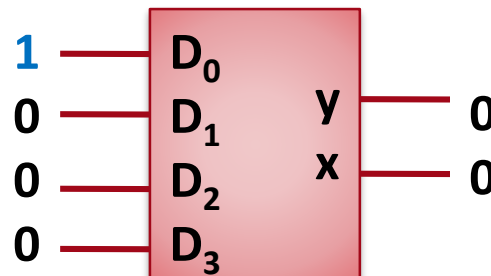- An encoder
 - It is a digital circuit that performs the inverse operation of a decoder
 - It has 2^n inputs lines and n output lines
- An example of an encoder is:
 - Octal-to-binary conversion, it has:
 - 8 inputs : the octal code and
 - 3 outputs : the corresponding binary number
- It is assumed that only one input has a value of 1 at any given time



OCTAL TO BINARY ENCODER

Table 4.7

Truth Table of an Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

- It can be implemented with 3 OR gates

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

- But, it has some limitations

OCTAL TO BINARY ENCODER:

LIMITATIONS

- This encoder has some limitations:
 1. It is assumed that only one input can be active at any given time,
 - If 2 inputs are active simultaneously, the output produces an undefined combination
 - **To resolve this** → higher priority with higher subscript
 2. A output with all 0's is generated when all the input are 0;
 - But this output is the same as when D0 is equal to 1
 - **To resolve this** → one more output is used to indicate whether at least one input is equal to 1.

How to design?
Know internal ?

PRIORITY ENCODER

- A *priority encoder* is an encoder circuit that overcomes the limitations of octal-to-binary encoder previously implemented.

Table 4.8
Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

How to design?
Know internal ?


PRIORITY ENCODER(CONT.)

D_0D_1 \ D_2D_3		D_2			
		00	01	11	10
D_0	00	m_0 X	m_1 1	m_3 1	m_2 1
	01	m_4	m_5 1	m_7 1	m_6 1
	11	m_{12}	m_{13} 1	m_{15} 1	m_{14} 1
	10	m_8	m_9 1	m_{11} 1	m_{10} 1

$$x = D_2 + D_3$$

D_0D_1 \ D_2D_3		D_2			
		00	01	11	10
D_0	00	m_0 X	m_1 1	m_3 1	m_2
	01	m_4 1	m_5 1	m_7 1	m_6
	11	m_{12} 1	m_{13} 1	m_{15} 1	m_{14}
	10	m_8	m_9 1	m_{11} 1	m_{10}

$$y = D_3 + D_1D'_2$$

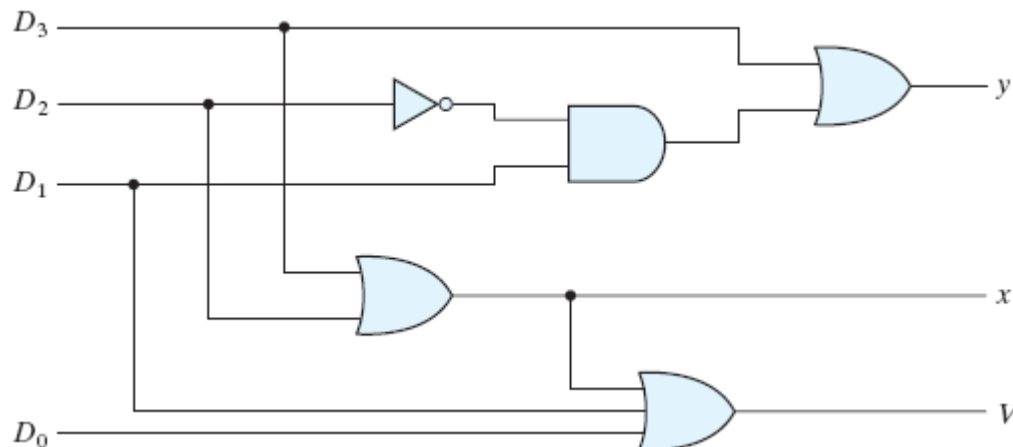


MULTIPLEXERS

- A multiplexer (MUX) is a combinational circuit that
 - selects binary information from one of many input lines and
 - directs it to a single output line.

- It is also called a *Data selector*

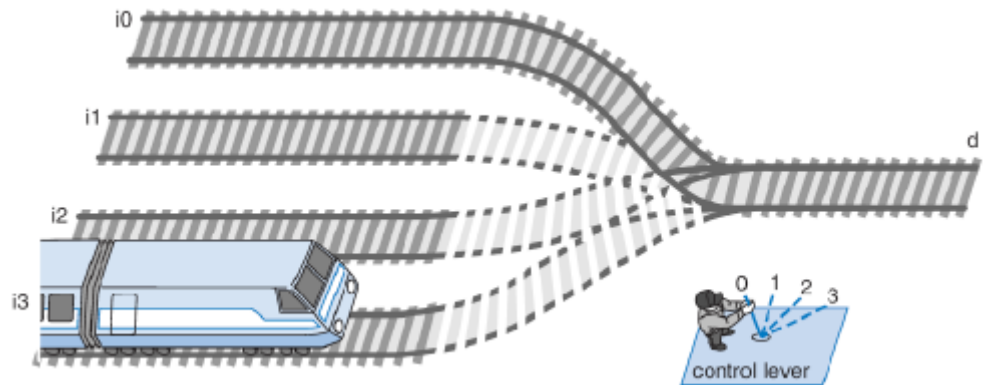- There are:
 - 2^n input lines
 - n selection lines whose bit combinations determine which input is selected, and
 - Single output




TWO-TO-ONE MULTIPLEXER

It has:


- 2 inputs, 1 selection and 1 output

S	Y
0	I_0
1	I_1

$$Y = S'I_0 + SI_1$$

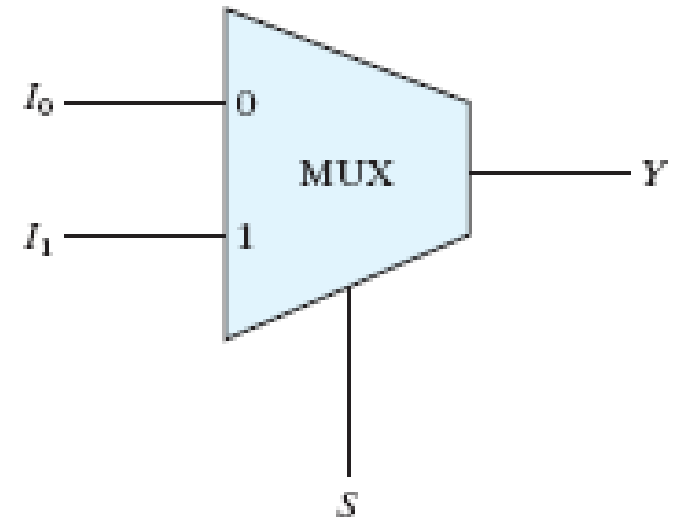

(b) Block diagram

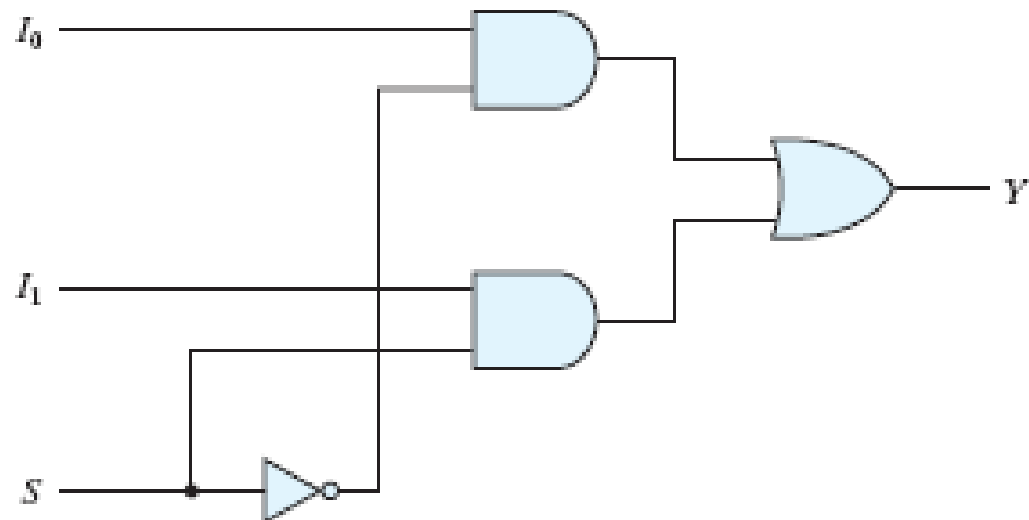

(a) Logic diagram

How to design?
Know internal ?



FOUR-TO-ONE MULTIPLEXER

It has:

- 4 inputs, 2 selection and 1 output

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3
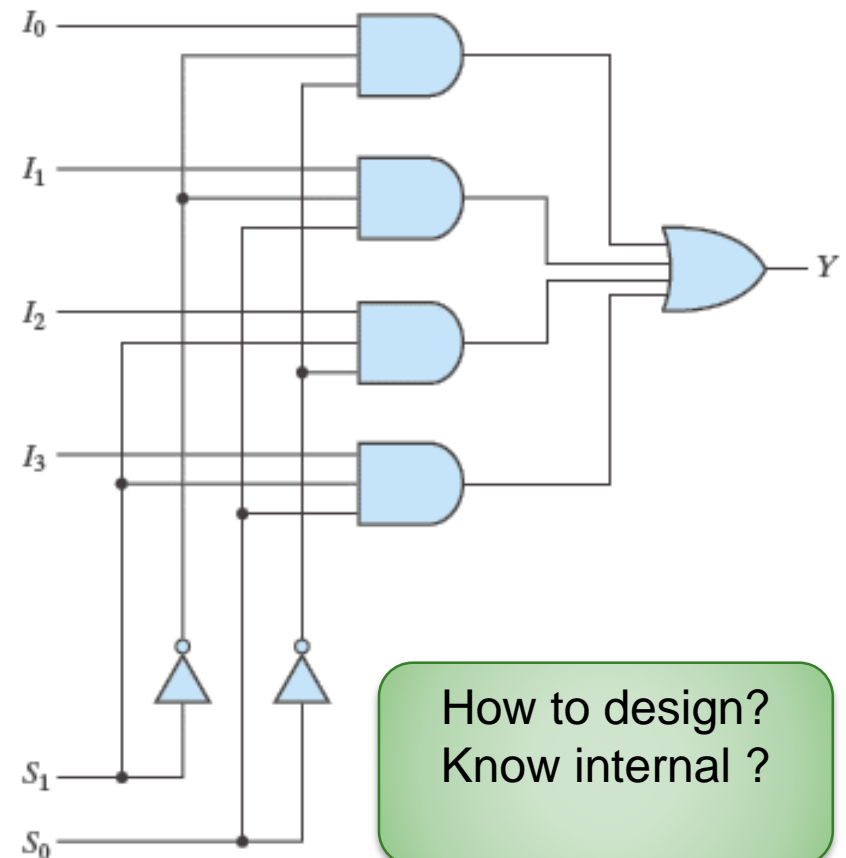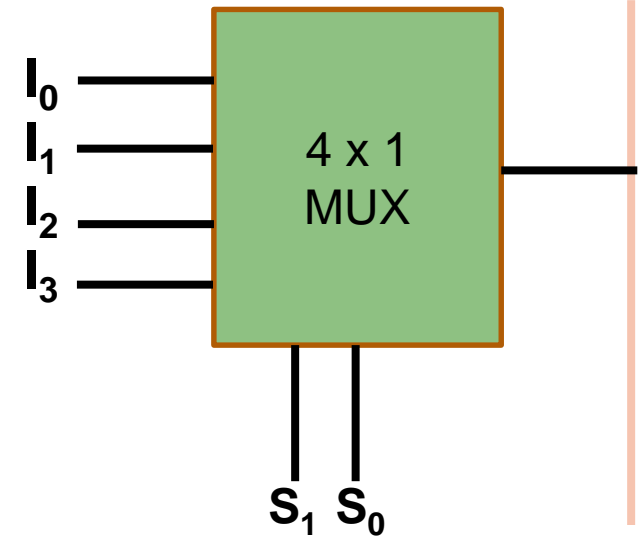
$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$




How to design?
Know internal ?

MULTIPLEXER WITH ENABLE INPUT

- As decoder, multiplexer may have an enable input:
 - When $E=0$, the outputs are disabled
 - When $E=1$, normal multiplexer

E	S1	S0	Y
0	x	X	All 0's
1	0	0	I_0
1	0	1	I_1
1	1	0	I_2
1	1	1	I_3

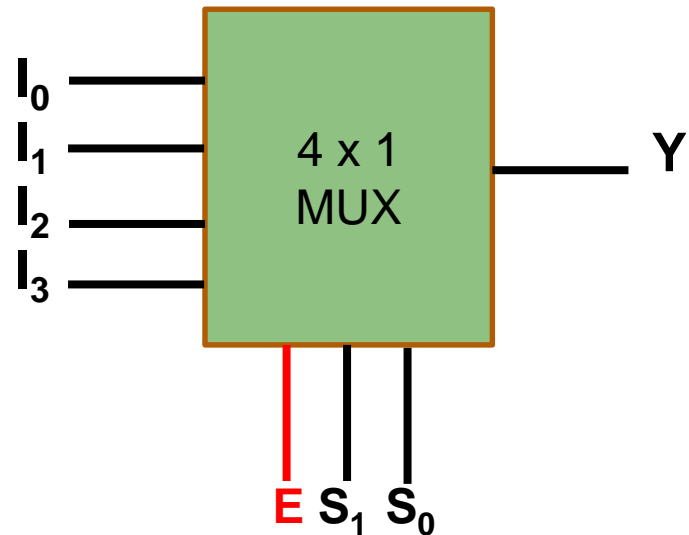

QUADRUPL 2-TO-1 LINE MULTIPLEXER

- The circuit has 4 MUXs,
 - Each MUX:
 - select one of two input lines: A_0 or B_0
 - Output Y_0
 - Selection line S selects one MUX from the 4 MUXs.
- It can be seen as a circuit that selects one of two 4-bit numbers
- The enable input E must be active for normal operation.

E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B

Function table

QUADRUPLER 2-TO-1 LINE MULTIPLEXER (CONT.)


- The unit is enabled when $E=0$

If $S=0$, the four A inputs have a path to the four outputs

If $S=1$, the four B inputs have a path to the four outputs

- When $E=1$, the outputs are all 0's regardless the value of S


E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B

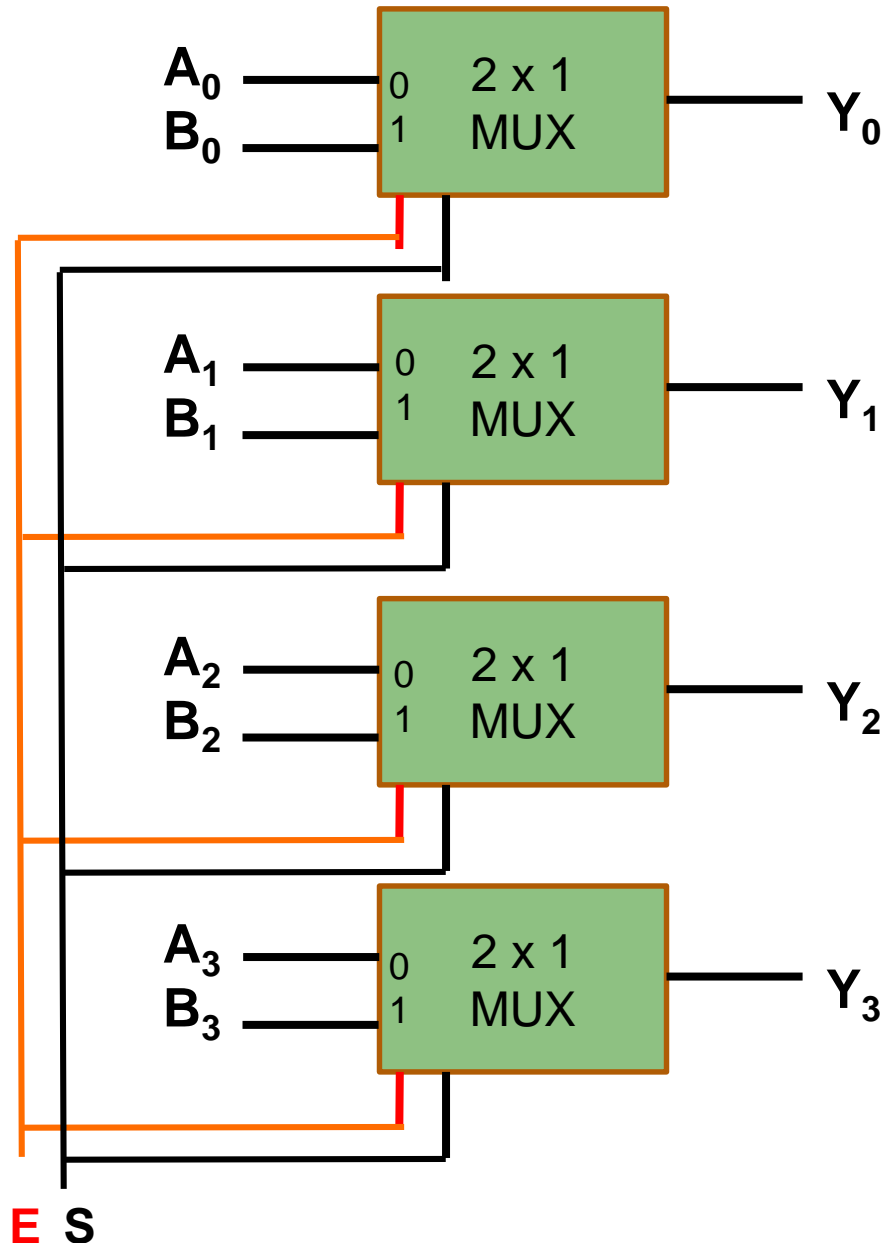

BOOLEAN FUNCTION IMPLEMENTATION

○ *Example 1:* $F(x,y,z)=\Sigma(1,2,6,7)$

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

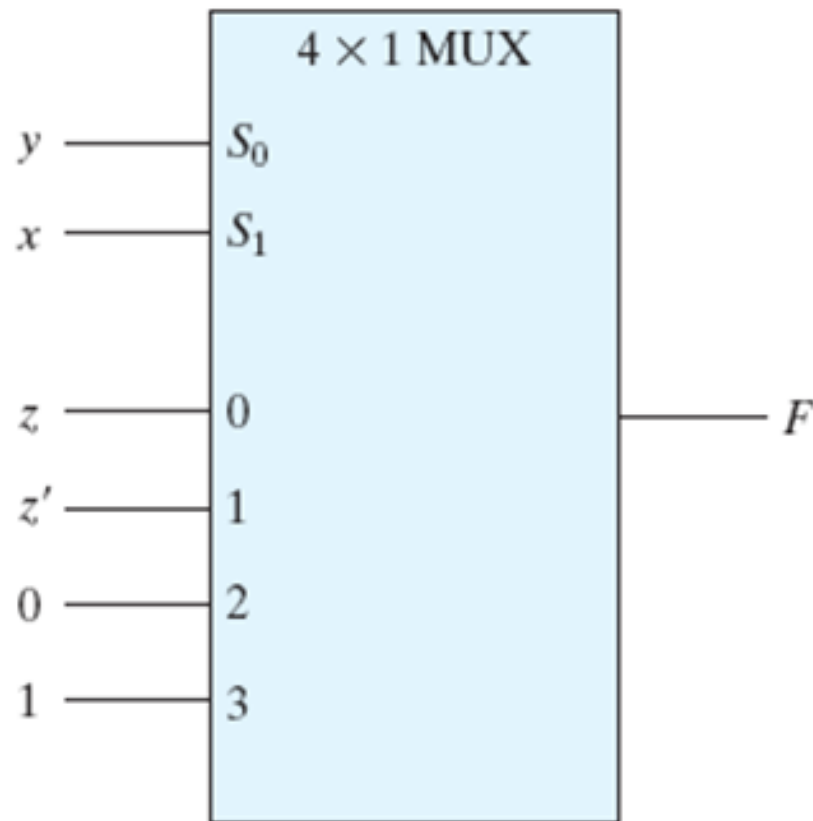


The first $n-1$ variables are applied to selection inputs and we evaluate the output as a function of the last variable

BOOLEAN FUNCTION IMPLEMENTATION (CONT.)

How to use as a
block

Example2: $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

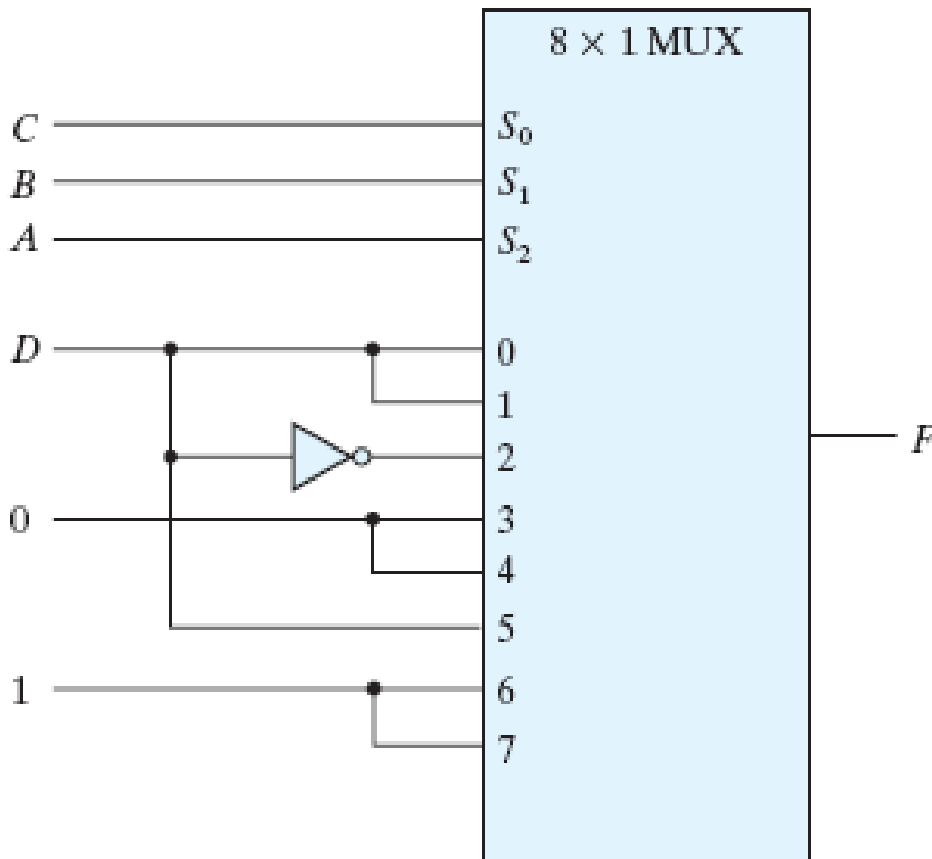

MULTIPLEXER WITH A DECODER

- A 2^n -to-1 line multiplexer is constructed from:
 - An n -to- 2^n decoder
 - AND gate for each 2^n input lines
 - An OR gate

try to solve it?

DEMULTIPLEXER

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Fig: 4.19

Demultiplexer is


A circuit that receives information from a single line and directs it to one of 2^n output lines.

The decoder with enable input can function as a demultiplexer.

The decoder in fig. 4.9 can function as 1-to-4 line demultiplexer, when:

- E is taken as data input
- A and B as selection inputs

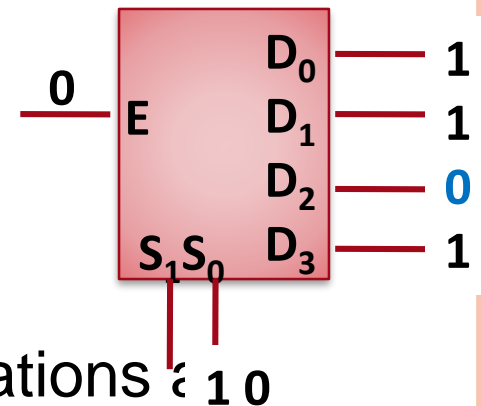Because decoder and demultiplexer operations obtained from the same circuit, a decoder with enable input is referred to as a *decoder-demultiplexer*





THANKS

We covered from:

Ch.4 (sec. 4.9→4.11)

Skip: three- state gates in sec. 4.11

Next lecture: Sequential circuits (latch & flip-flop)