




CS 221 LOGIC DESIGN

Fall 2021

By Wessam El-Behaidy & Salwa Osama

1

 

2

REGISTERS & COUNTERS

Lecture 9

SEQUENTIAL CIRCUIT


- A circuit with flip-flops is considered a sequential circuit even in the absence of combinational gates
- Circuits that include flip-flops are usually classified by the function they perform rather than by the name of the sequential circuit.
- Two such circuits are **registers** and **counters**

REGISTER

- A *register* is a group of flip-flops.
- An *n-bit* register consists of:
 - A group of n flip-flops capable of storing n bits of binary information
- Its broadest definition,
 - A register consists of a group of flip-flops together with gates that affect their operation.
 - Flip-flops hold the binary information and
 - The gates determine how the information is transferred into the register

SIMPLEST REGISTER

 - 4-bit register consists of only 4 D-type flip-flops
 - Common clock input triggers all flip-flops on the positive edge
 - When input **Clear (Reset)** goes to active low (zero) → all flip-flops are reset asynchronously.
 - R inputs must be at logic 1 during normal clocked operation



4-bit register

REGISTER WITH PARALLEL LOAD

- The transfer of new information into a register is referred to as *loading* or *updating* the register
- If all the bits of the register are loaded simultaneously with a common clock pulse, we say *loading* is done in *parallel*.
- Previous 4-bit register (fig.6.1) will load the 4 inputs in parallel
 - A problem , with this configuration, is when the contents of the register must be unchanged.

BASIC COMPUTER REGISTERS

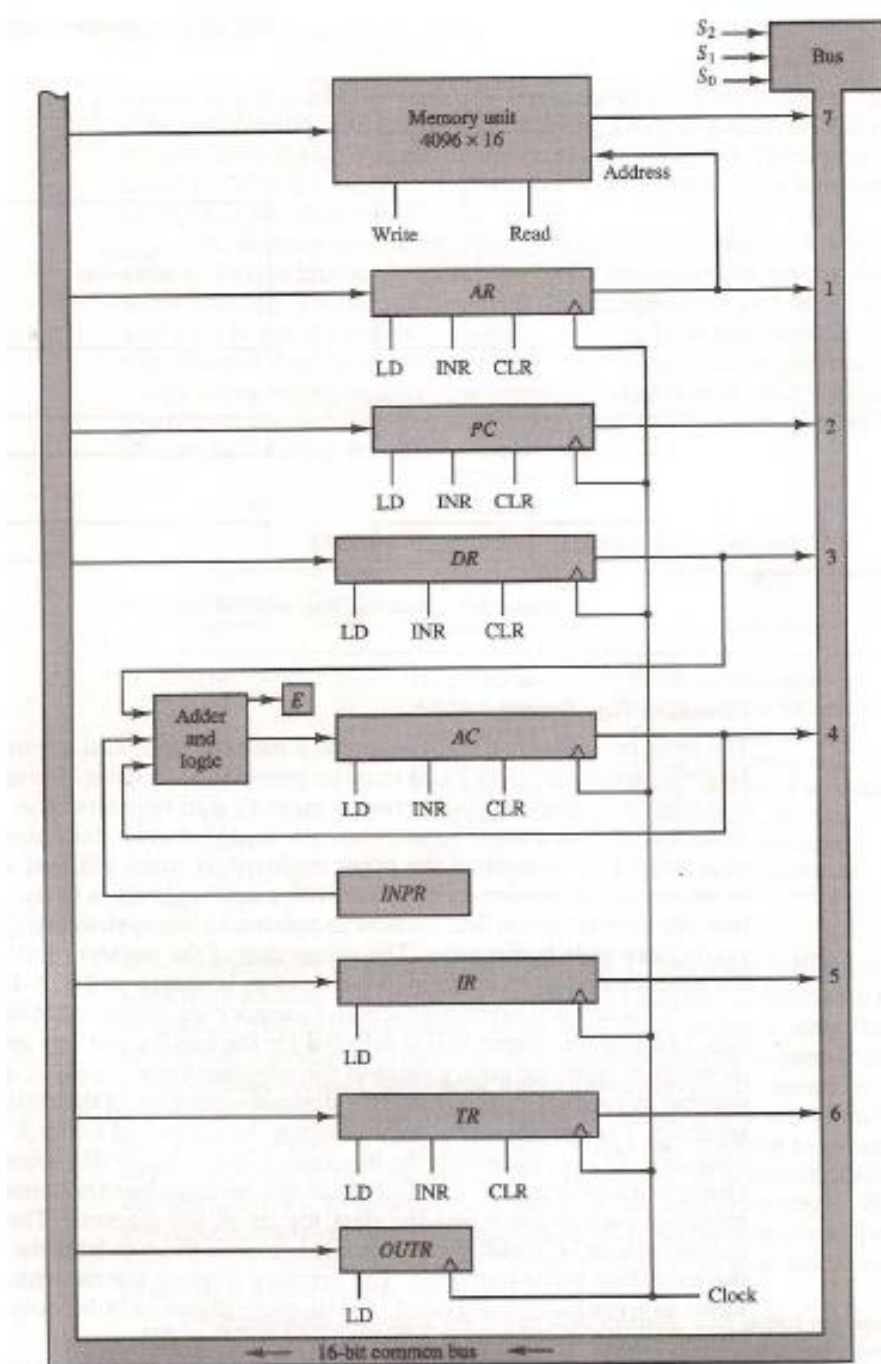


Figure 5-4 Basic computer registers connected to a common bus.

REGISTER WITH PARALLEL LOAD (CONT.)

- Unchanged the content of the 4-bit register needs:
 - a) The inputs must be held constant
 - ➔ the data bus would be unavailable for other traffic
 - b) The clock must be inhibited from reaching the register by controlling the clock input signal with an enabling gate
 - ➔ inserting gates into the clock path is ill advised because it produces uneven propagation delays between the master clock and the inputs of flip-flops

To fully synchronize the system, we must ensure that all clock pulses arrive at the same time anywhere in the system, so that all flip-flops trigger simultaneously

MASTER CLOCK GENERATOR & CONTROL SIGNAL

○ *Master clock generator*

- It supplies a continuous train of clock pulses
- The pulses are applied to all flip-flops and registers in the system

○ *Control Signal*

- A separate *control signal* must be used to decide which register operation will execute at each clock pulse

REGISTER WITH PARALLEL LOAD (CONT.)



- For this reason, it is advisable to:
 - control the operation of the register with the D inputs
- A 4-bit register with a load control input
 - The load input determines the action to be taken with each clock pulse
 - When load =1, four external inputs are transferred into register with next positive transition
 - When load =0, the output of the flip-flops are connected to their respective inputs (“no change” condition)

| L(oad) | D _A |
|--------|----------------|
| 0 | A(t) |
| 1 | I(nputs) |

REGISTER WITH PARALLEL LOAD (CONT.)

| L(oad) | D_A |
|--------|----------|
| 0 | $A(t)$ |
| 1 | I(nputs) |


$$D_A = L'A + LI$$

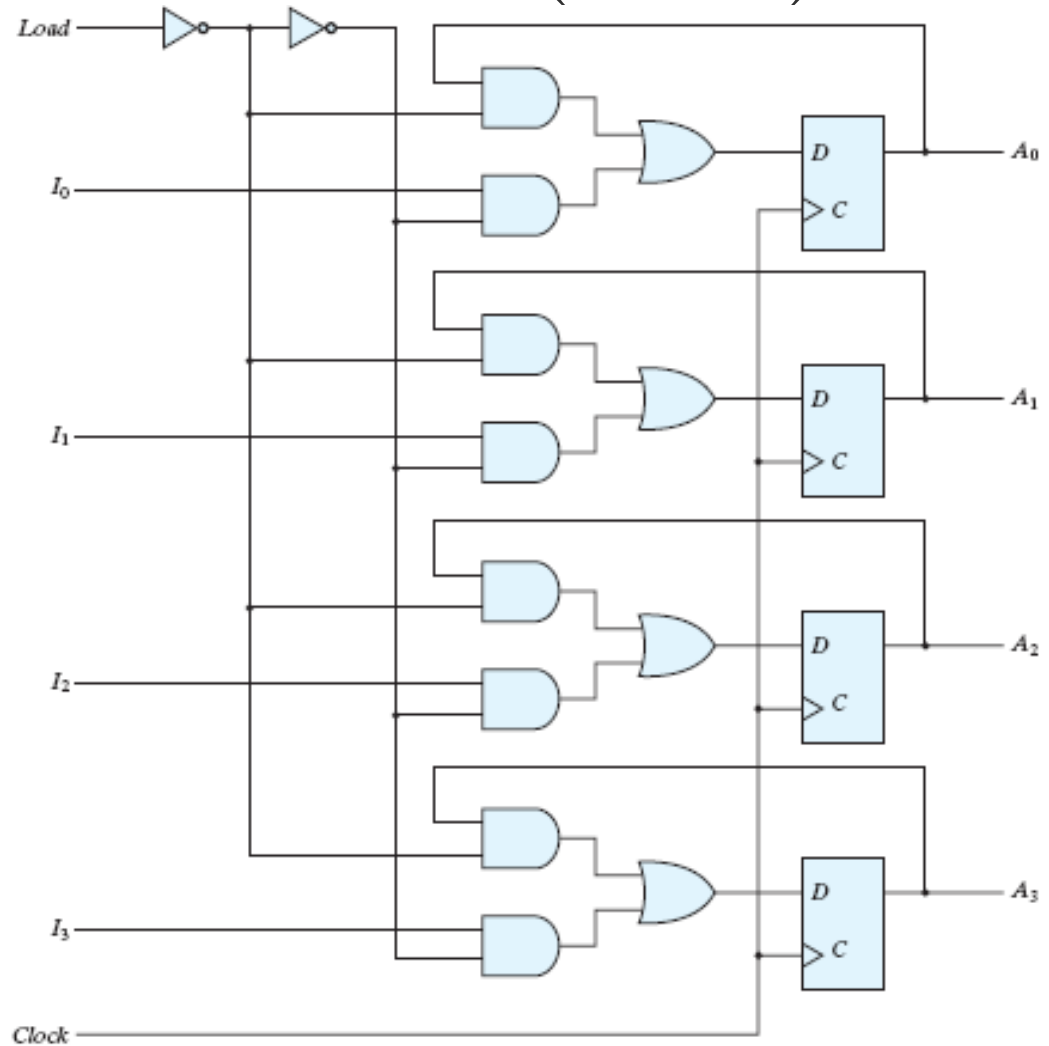 


REGISTER WITH PARALLEL LOAD (CONT.)

- The additional gates implement:
- A 2 x 1 Mux whose output drives the input to the register with either:
 - the data bus or the output of the register

$$D_A = L'A + LI$$

 

(a) Logic diagram

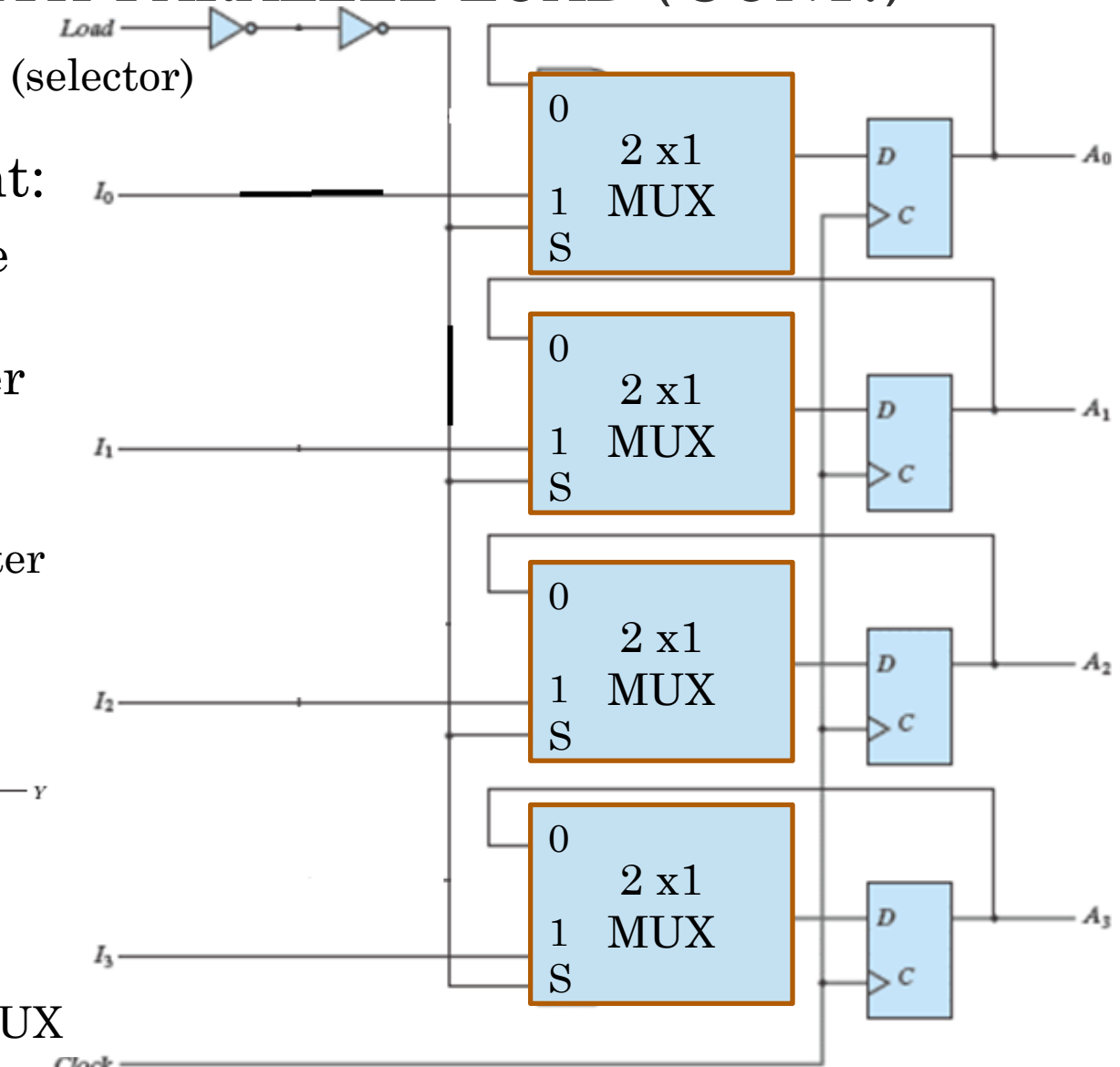

Internal design of 2x1 MUX

SHIFT REGISTER

- A register capable of shifting the binary information held in each cell to its neighboring cell, in a selected direction
- The logical configuration of a shift register:
 - A chain of flip-flops in cascade, with the output of one flip-flop connected to the input to the next flip-flop

SHIFT REGISTER (CONT.)

- The simplest shift register, shown in fig. 6.3
 - This shift is unidirectional
 - Each clock pulse shifts the contents of the register one bit position to the right
 - Serial input (SI): determines what goes into the leftmost flip-flop
 - Serial output (SO): is the output from the rightmost flip-flop

 


fig. 6.3: 4-bit shift register

SERIAL & PARALLEL MODE

Serial Mode

The register have a single serial output.

Information is transferred one bit at a time while the registers are shifted in the same direction

Parallel Mode


Information is available from all bits of a register and

all bits can be transferred simultaneously during one clock pulse


SERIAL TRANSFER FROM REGISTER A TO B

To prevent loss of information stored in source register

In practice can be problematic

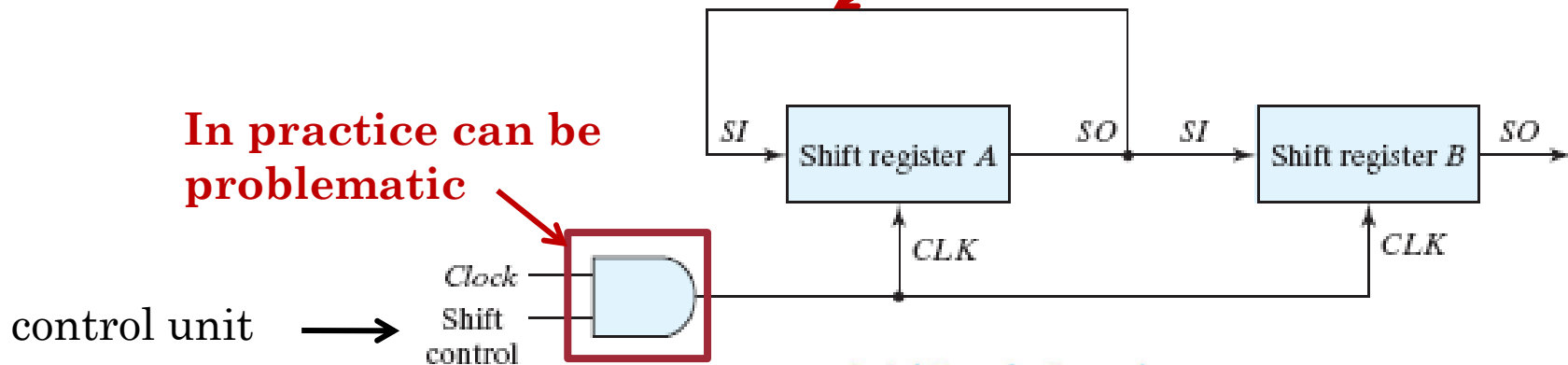


Serial-Transfer Example

 



| Timing Pulse | Shift Register A | | | | Shift Register B | | | |
|---------------|------------------|---|---|---|------------------|---|---|---|
| Initial value | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| After T_1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| After T_2 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| After T_3 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| After T_4 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 |

UNIVERSAL SHIFT REGISTER

 

- It has the following capabilities:
 - A *clear* control to clear the register to 0
 - A *clock* input to synchronize the operations
 - A *shift-right* control to enable the shift-right operation and the serial input and output lines associated with the shift right
 - A *shift-left* control to enable the shift-left operation and the serial input and output lines associated with the shift left
 - A *parallel-load* control to enable a parallel transfer and the n input lines associated with the parallel transfer
 - n parallel output lines
 - A *control state* that leaves the information in the register unchanged in response to the clock.

4-BIT UNIVERSAL SHIFT REGISTER

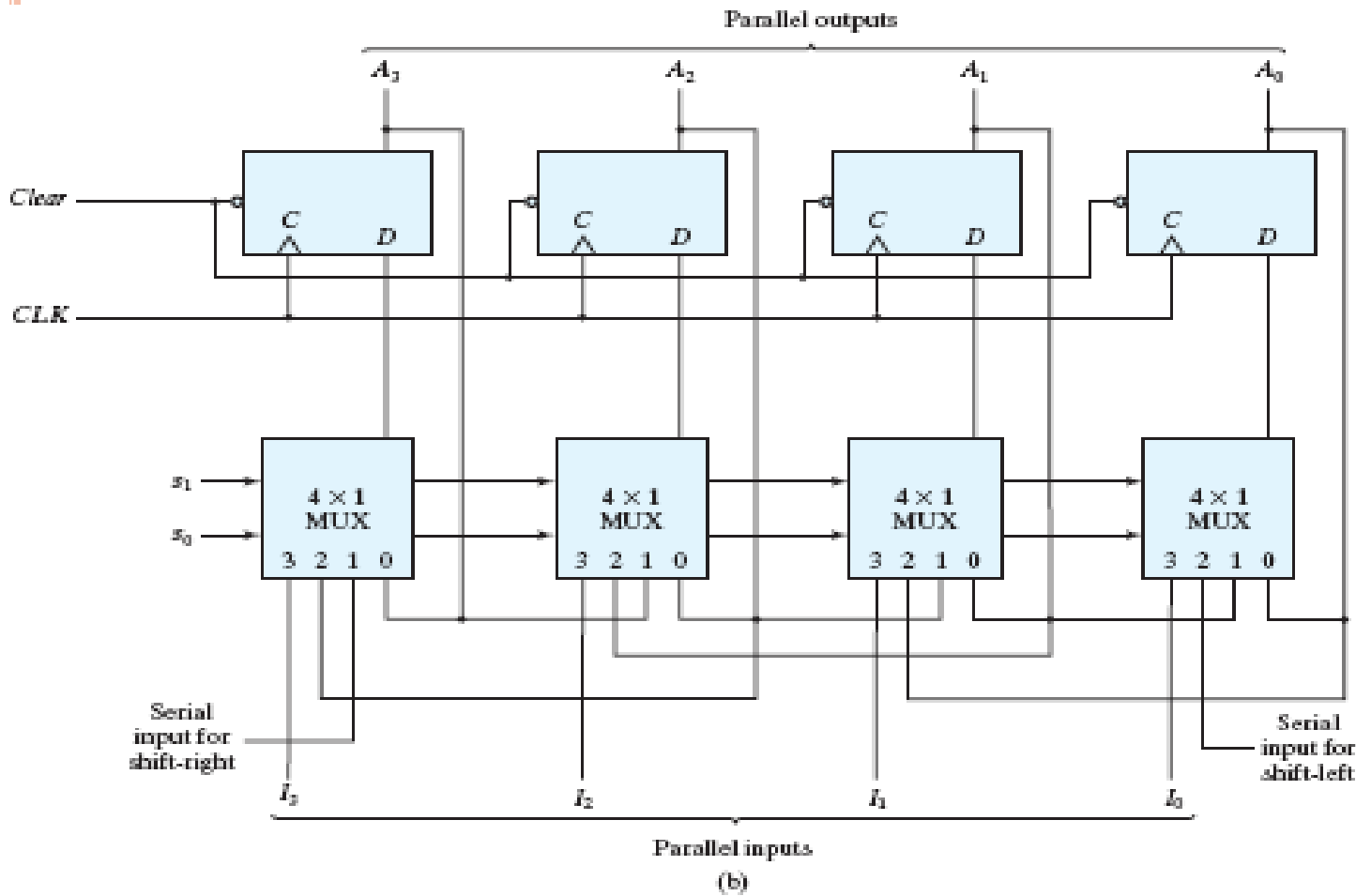 

Mode Control

| s_1 | s_0 | Register Operation |
|-------|-------|--------------------|
| 0 | 0 | No change |
| 0 | 1 | Shift right |
| 1 | 0 | Shift left |
| 1 | 1 | Parallel load |

PARALLEL-TO-SERIAL & SERIAL-TO-PARALLEL CONVERSION

- Shift register are often used to interface digital systems situated remotely from each other

Ex: to transmit an n bits between 2 points

- If the distance is far,
 - ➔ it will be expensive to transmit n -bit in parallel
 - ➔ it is economical to use a single line and transmit the information serially
- ***The transmitter:***
 - Accepts the n -bit data in parallel into a shift register and transmit it serially. “parallel to serial conversion”
- ***The receiver:***
 - Accepts the data serially into a shift register.
 - When all n -bits are received, they are taken from the output of the register in parallel. “serial-to-parallel conversion”

COUNTER


- A *counter* is essentially a register (*special type of register*) that goes through a predetermined sequence of binary states.
- The gates in the counter are connected in such a way as to produce the prescribed sequence of states.
- Counters are available in 2 categories:
 - Ripple counters
 - C input of some or all flip-flops are triggered, not by the common clock , but rather by the transition occurs in other flip-flop outputs.
 - Synchronous counters
 - C input of all flip-flops receive common clock

COUNTDOWN BINARY COUNTER

- It's the reverse of up binary counter
- It counts from 1111 to 0000 and back to 1111
- Its procedure:
 - The least significant position is complemented with each pulse
 - A bit in any other position is complemented if all lower significant bits are equal to 0
- ➔ Its design is as count up except that the inputs to the AND gates must come from the complemented outputs (A' s), not normal outputs (A s)


UP-DOWN BINARY COUNTER

| Up | Down | Operation |
|----|------|-------------|
| 0 | 0 | No change |
| 1 | x | Counts up |
| 0 | 1 | Counts down |

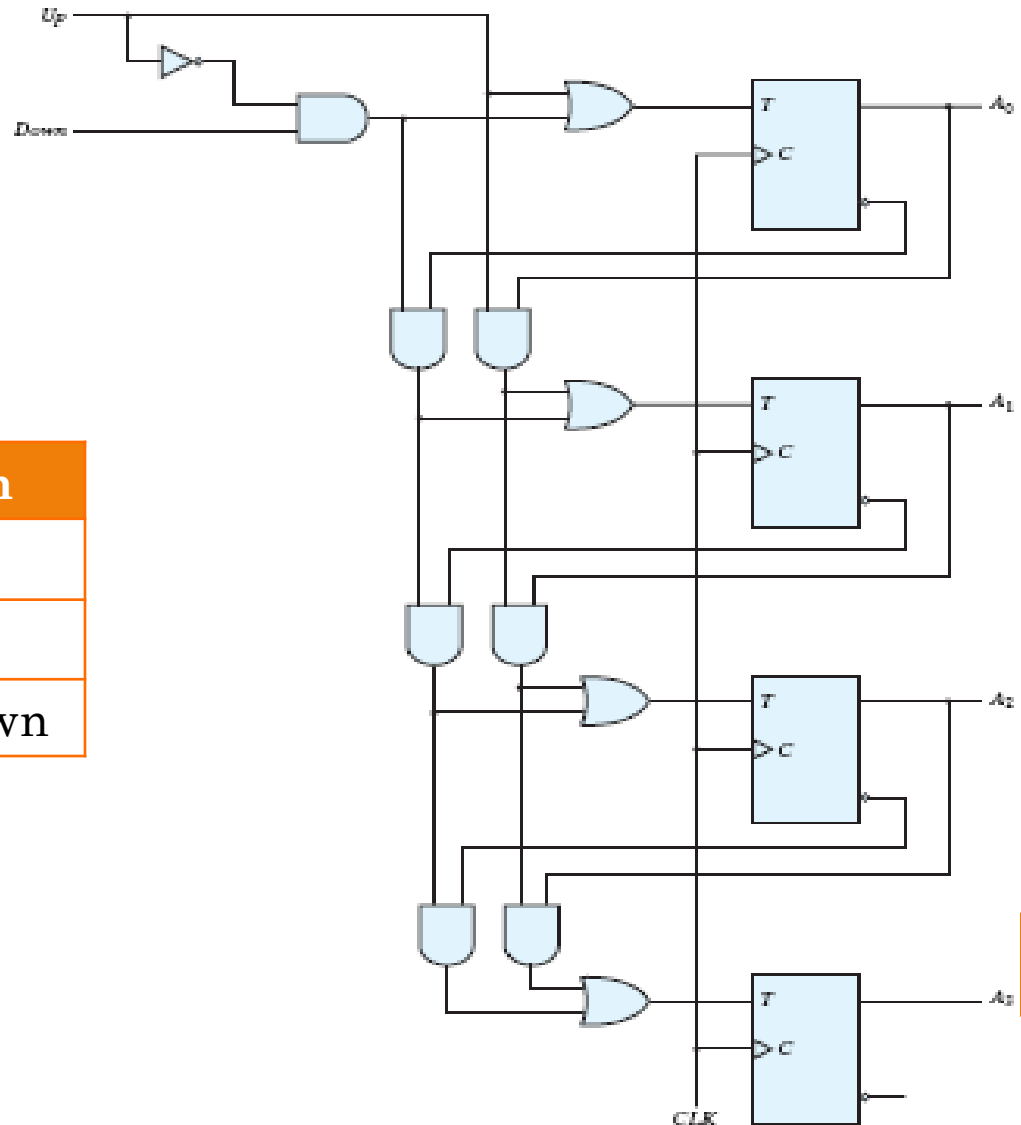

BINARY COUNTER WITH PARALLEL LOAD

 
- Counters often required a parallel load capability for transferring an initial binary number into the counter prior to count.



BINARY COUNTER WITH PARALLEL LOAD CONT.)

Function Table for the Counter of Fig. 6.14

| Clear | CLK | Load | Count | Function |
|-------|-----|------|-------|-------------------------|
| 0 | X | X | X | Clear to 0 |
| 1 | ↑ | 1 | X | Load inputs |
| 1 | ↑ | 0 | 1 | Count next binary state |
| 1 | ↑ | 0 | 0 | No change |

 

Reduce delay for generating the carry



THANKS